

# Computer Organization, Spring 2019

## Lab 1: 32-bit ALU

**Due: 2019/04/11**

### 1. Goal

The goal of this LAB is to implement a 32-bit ALU (Arithmetic Logic Unit). ALU is the basic computing component of a CPU. Its operations include AND, OR, addition, subtraction, etc. This LAB will help you understand the CPU architecture. LAB 1 will be reused; you will use this module in later LABs. The function of testbench is to read input data automatically and output erroneous data. Please unzip the files in the same folder.

### 2. HW Requirement

- Please use ModelSim as your HDL simulator.
- Please attach **student IDs** as a comment at the top of each file.
- PLEASE FOLLOW THE FOLLOWING RULE!** Zip your folder and submit only one \*.zip file. Name the \*.zip file with your student IDs (e.g., 0616001\_0616002.zip). Other filenames and formats such as \*.rar and \*.7z are NOT accepted! Multiple submissions are accepted, and the version with the latest time stamp will be graded. For the ease of grading, a team's submissions should be uploaded by the same person (so we don't have to check if your teammate submits a new/different version).
- Testbench module is provided.
- Any work by fraud will absolutely get a zero point.
- The names of top module and IO ports must be named as follows:**

Top module: alu.v

```
module alu (  
    rst_n,           // negative reset (input)  
    src1,            // 32 bits source 1 (input)  
    src2,            // 32 bits source 2 (input)  
    ALU_control,     // 4 bits ALU control input (input)  
    result,          // 32 bits result (output)  
    zero,            // 1 bit when the output is 0, zero must be set (output)  
    cout,            // 1 bit carry out (output)  
    overflow         // 1 bit overflow (output)  
);
```

ALU starts to work when the signal rst\_n is 1, and then catches the data from src1 and

src2. In order to have a good coding style, please obey the rules below:

- . One module in one file.
- . Module name and file name must be the same.

For example: The file "alu.v" only contains the module "alu".

g. instruction set: basic operation instruction (60%)

ALU action	Name	ALU control input
<b>And</b>	<b>And</b>	<b>0000</b>
<b>Or</b>	<b>Or</b>	<b>0001</b>
<b>Add</b>	<b>Addition</b>	<b>0010</b>
<b>Sub</b>	<b>Subtract</b>	<b>0110</b>
<b>Nor</b>	<b>Nor</b>	<b>1100</b>
<b>Nand</b>	<b>Nand</b>	<b>1101</b>
<b>Slt</b>	<b>Set less than</b>	<b>0111</b>

zcv three control signal : zero 、 carry out 、 overflow (30%)


zero must be set when the result is 0.

cout must be set when there is a carry out.


overflow must be set when overflow.

### 3. Architecture diagram

1-bit ALU (Top)

 

32-bit ALU

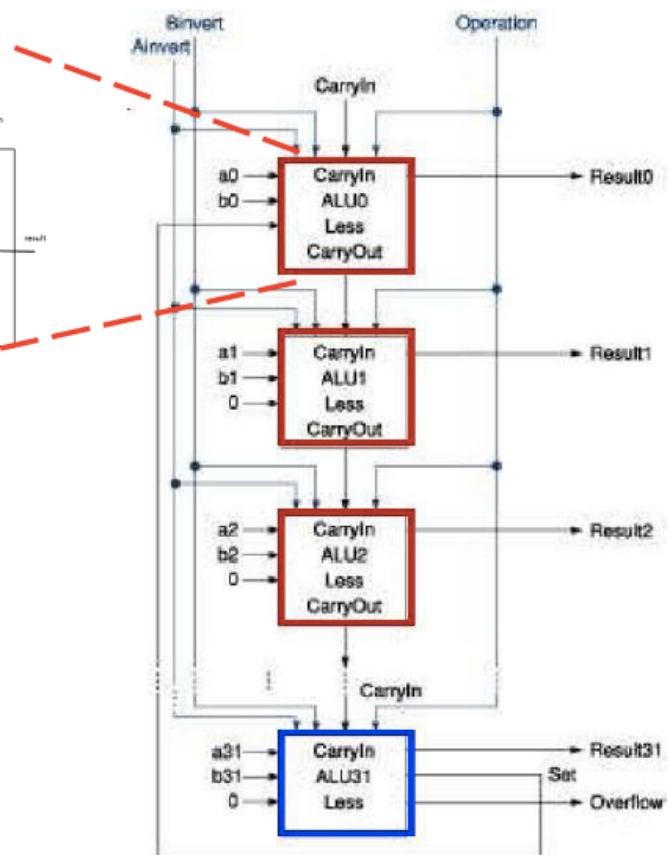


Blue frame is 1-bit ALU (Bottom)

#### 4. Bonus: Extra instruction set, will get extra score if you do successfully ◦ (10%)

ALU action	Name	ALU control input
Slt	Set less than	0111_000
Sgt	Set great than	0111_001
Sle	Set less equal	0111_010
Sge	Set great equal	0111_011
Seq	Set equal	0111_110
Sne	Set not equal	0111_100

Hint: Add a module named Compare in 1-bit ALU, it needs extra 3-bit control input – Compare\_sel.

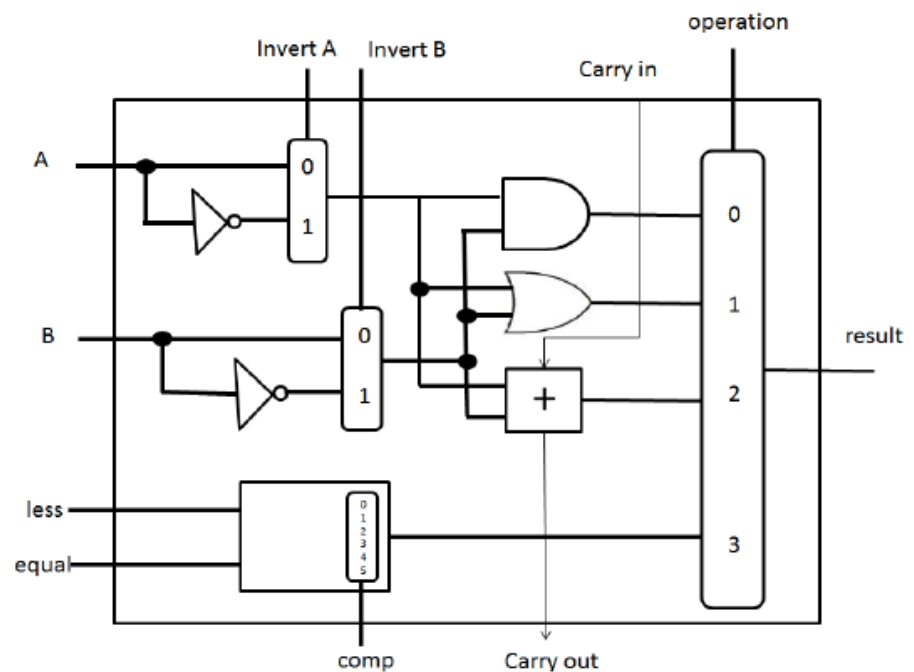Here is a reference architecture diagram.



#### 5. Grade

- Total: 110 points (plagiarism will get 0 point)
- Document: 10 points
- Late submission: 10 points off per day